

# UNIVERSITY OF ALASKA FAIRBANKS

## Department of Electrical and Computer Engineering

### INTRODUCTION TO ELECTRICAL AND COMPUTER ENGINEERING

EE F102-F01  
CRN: 32862

SPRING  
2023

## LECTURE 6

Monday  
06 FEB 2023  
DU 252  
09:15 – 10:15


Instructor  
**MAHER AL-BADRI**

# Outline

- ➔ BASIC LAWS (II)
- ➔ PARALLEL AND SERIES CIRCUITS
- ➔ MEASURING CURRENT AND VOLTAGE
- ➔ CIRCUIT ANALYSIS
- ➔ SOURCES
- ➔ EXAMPLE PROBLEMS

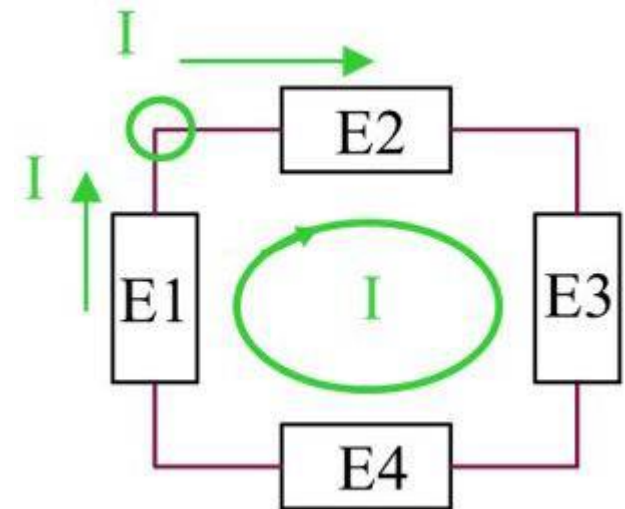
## Parallel and Series Circuits

Two branches are in **series** if they are connected by a **single node** and **no other branch is connected to that same node**.


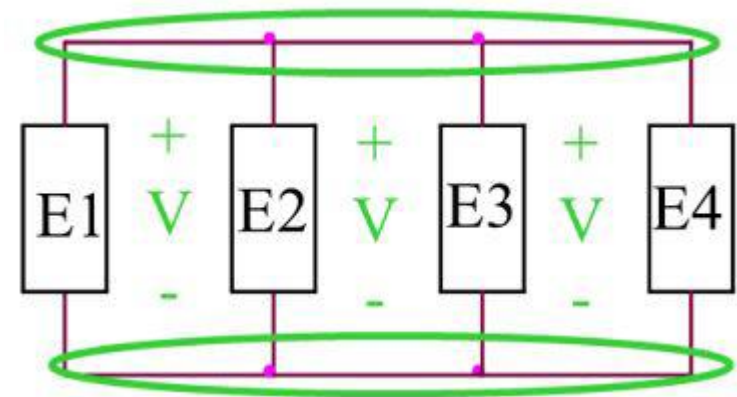
# Parallel and Series Circuits


Two branches are in **parallel** if they are connected directly to the **same two nodes**.


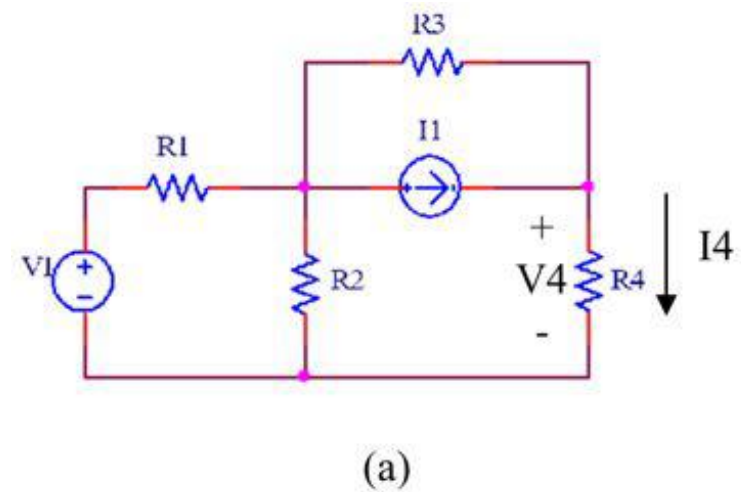
## Measuring Current and Voltage

In the circuit shown, we want to **measure the current  $I_4$  through  $R_4$** .


In order to make this measurement **the charge (current) needs to pass through the ammeter**.


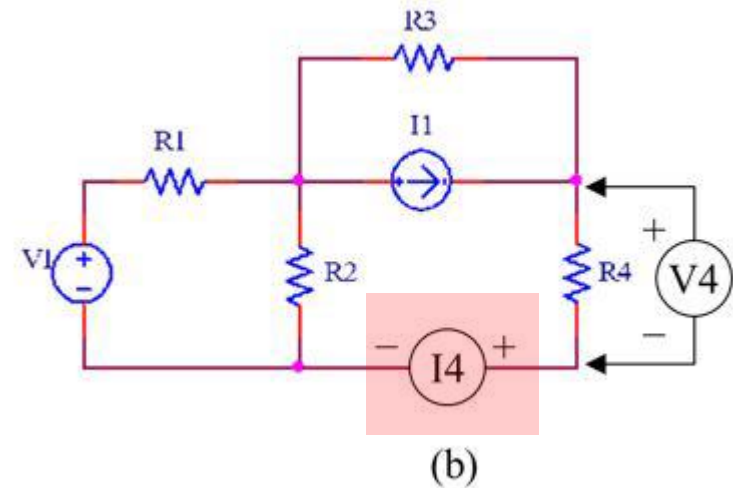
# Measuring Current and Voltage

Physically, the **circuit must be broken in the path of the desired current and an ammeter put in-line with that path** as shown.


The polarization of the ammeter must be in passive sign convention **with the desired current direction**.


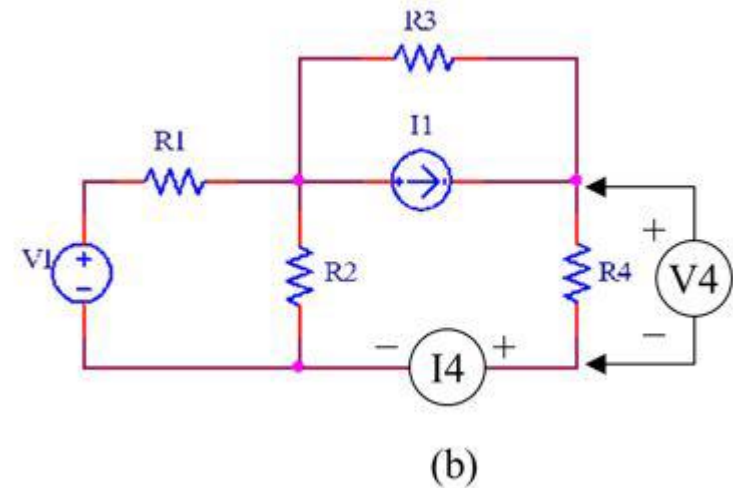
## Measuring Current and Voltage

Any **voltage drop across the ammeter** will change the measured current.

In this class we will assume an **ideal ammeter with zero internal resistance**, so the voltage drop across the meter is **zero**.




## Measuring Current and Voltage

We would also like to **measure the voltage across  $R_4$** .

We need to put the meter **in parallel** with  $R_4$ .

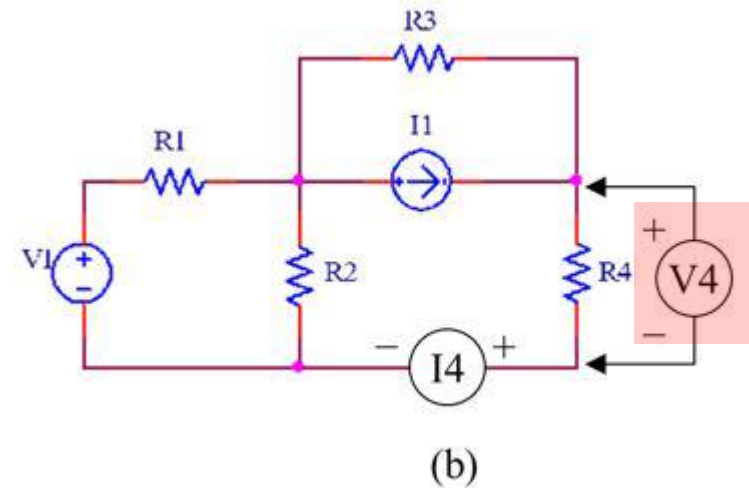
We need to connect the voltmeter across  $R_4$  in the **same polarity** of the desired measurement.




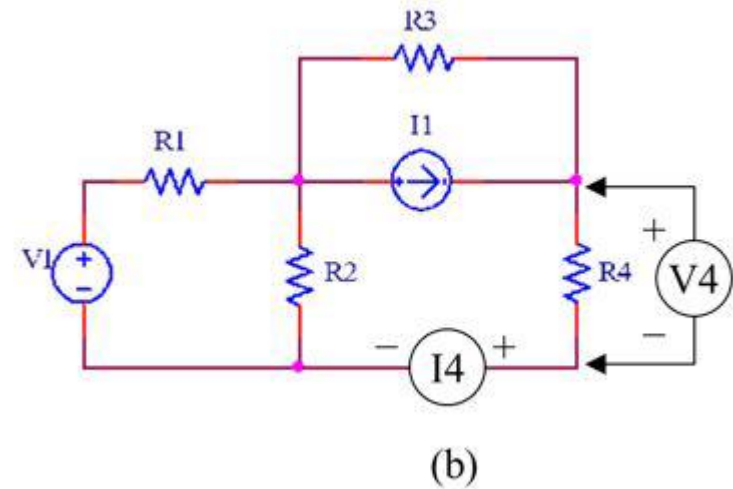
# Measuring Current and Voltage


In this class we will assume an **ideal voltmeter with infinite internal resistance**, so the current passing through (leaking) the meter will be **zero**.


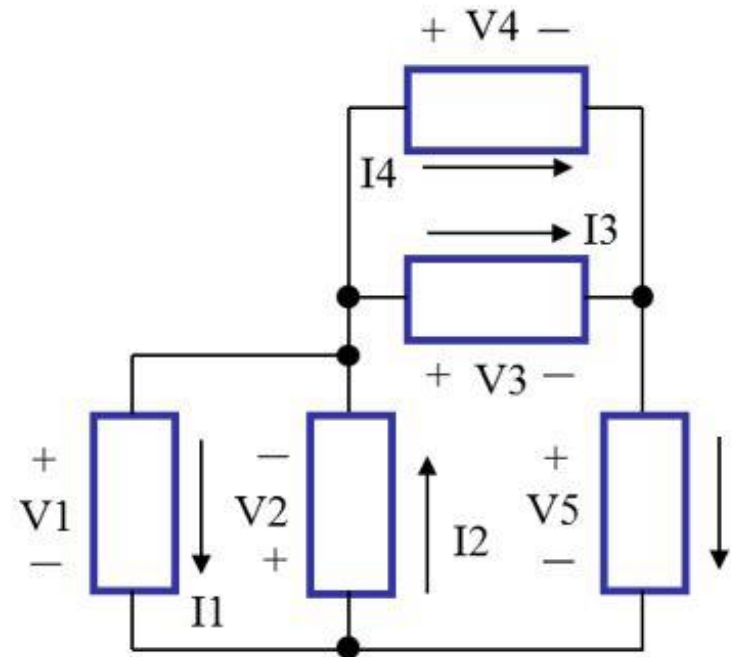
# Circuit Analysis

Circuit analysis is based on laws.


It is used to solve for **unknown voltages and currents** from which all other variables can be derived.



# Circuit Analysis


For the circuit shown, we would like to determine all **currents** through and **voltages** across all elements in the circuit.

**Where do we start?**

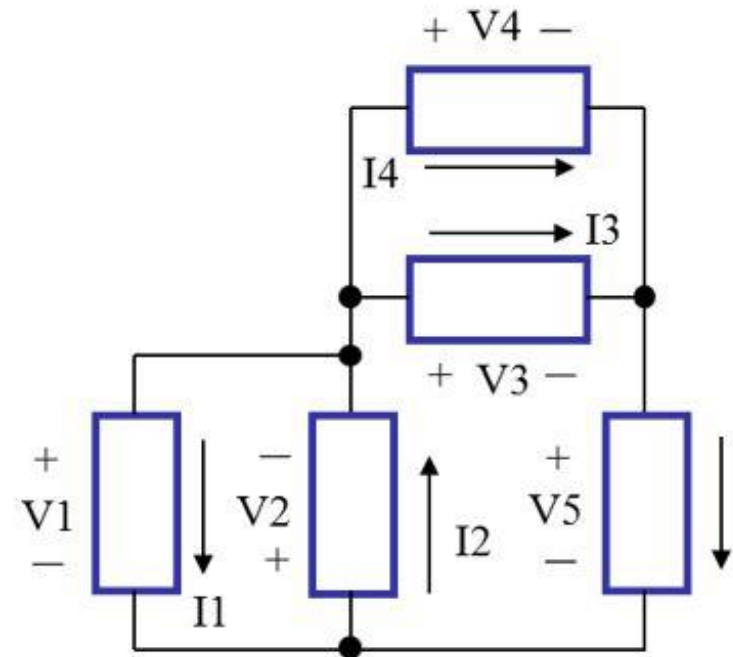


# Circuit Analysis

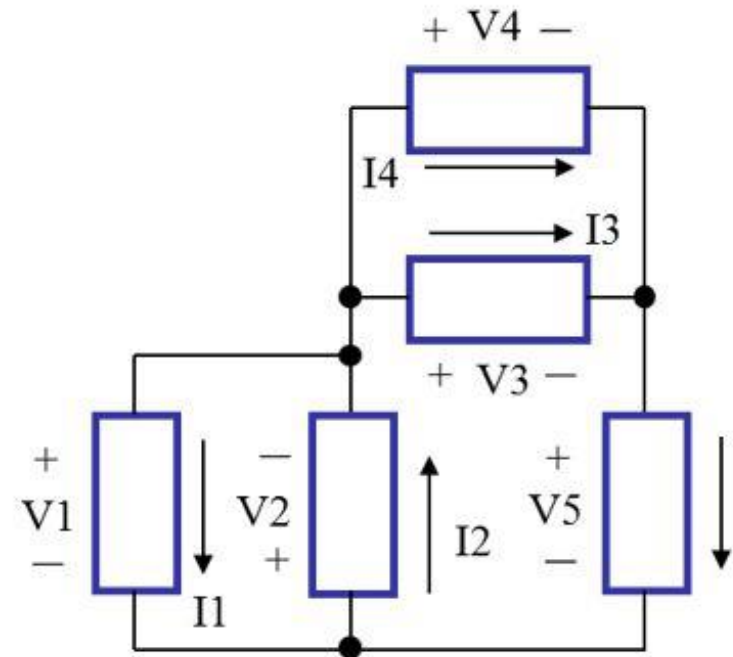1. **Arbitrarily** choose **either** the **voltage polarity** or **current directions** for the measured voltages or currents.




# Circuit Analysis

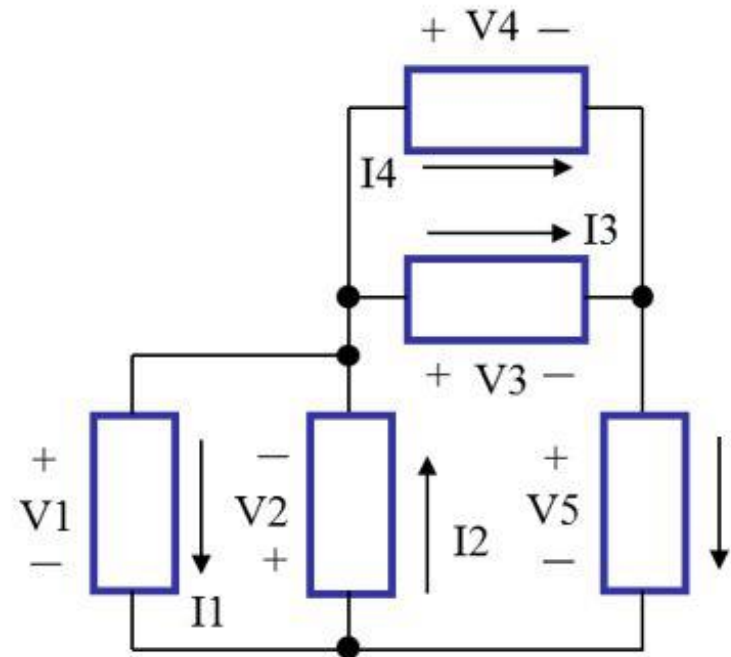2. Use **passive sign convention** to specify the required measured current direction or voltage polarity for the measurement not specified in Step 1.



# Circuit Analysis

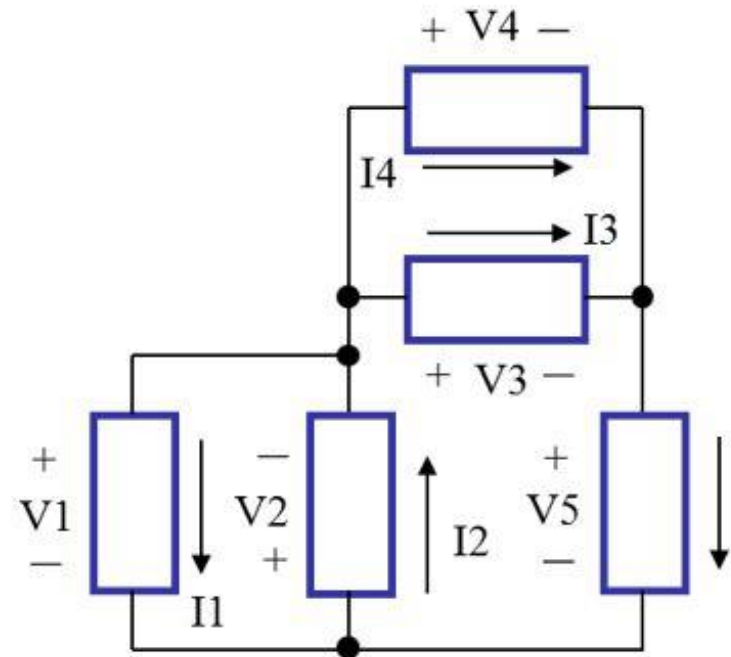3. Apply **KVL** and/or **KCL** and/or **conservation of energy** to solve for all unknowns.




# Sources
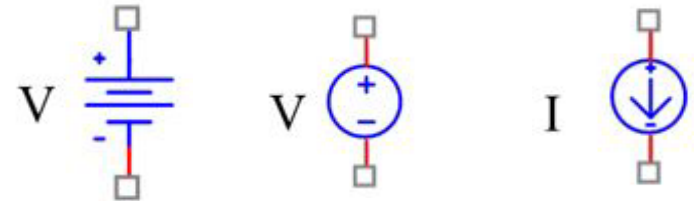
## Ideal Independent Sources




The figure shows some symbols for **direct current** or **DC sources**.

The two on the left are **voltage sources** and the one on the right is a **current source**.


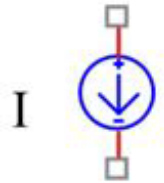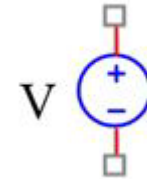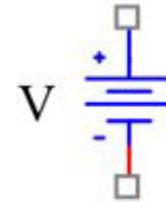
# Sources




An **ideal voltage source** provides a constant voltage across its terminals (regardless the value of current).




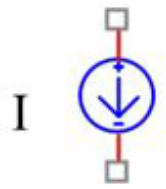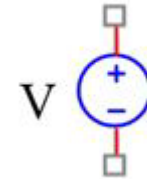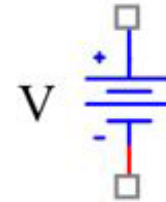
## Sources

An **ideal current source** provides a constant current passing through it (regardless the value of voltage).







# Sources
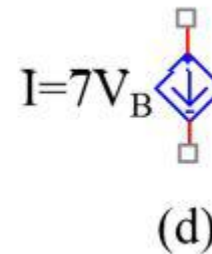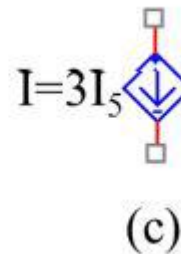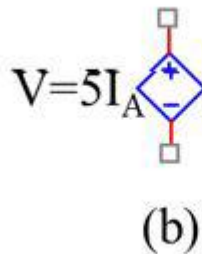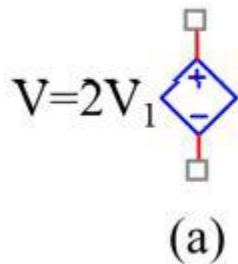
## Ideal Dependent Sources

A **dependent source** can be either a voltage source or a current source.

The output of a dependent source is controlled by a voltage or current which exist in a different part of the circuit.







# Sources

## Ideal Dependent Sources

There are four different types of dependent sources:

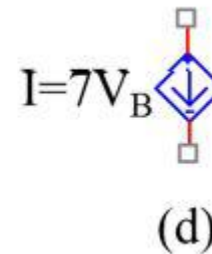
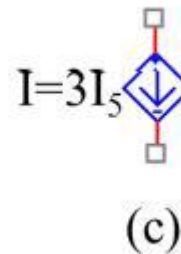
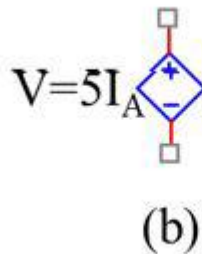
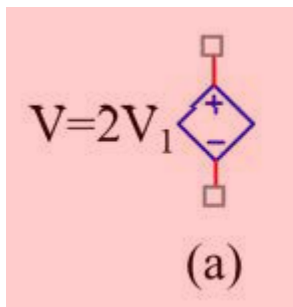
### (a) Voltage Controlled Voltage Source



# Sources

## Ideal Dependent Sources

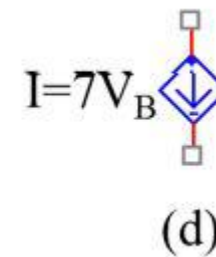
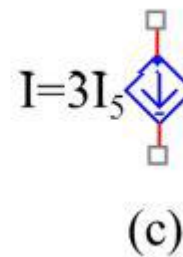
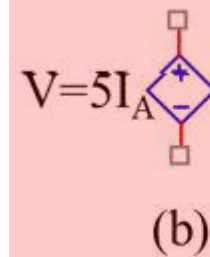
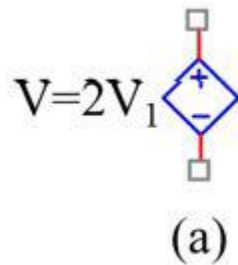
### (b) Current Controlled Voltage Source



# Sources

## Ideal Dependent Sources

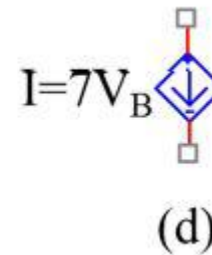
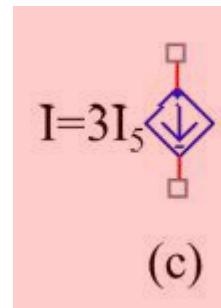
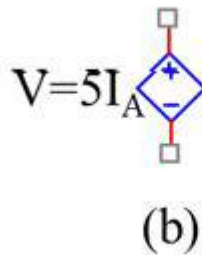
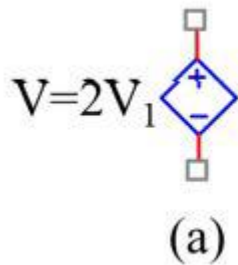
### (c) Current Controlled Current Source



# Sources

## Ideal Dependent Sources
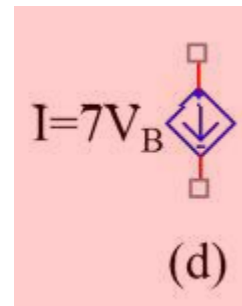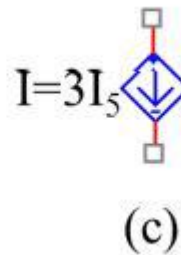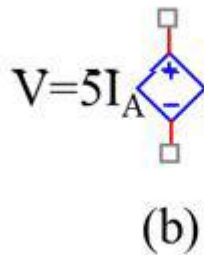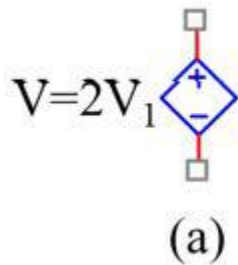
### (d) Voltage Controlled Current Source







# Sources
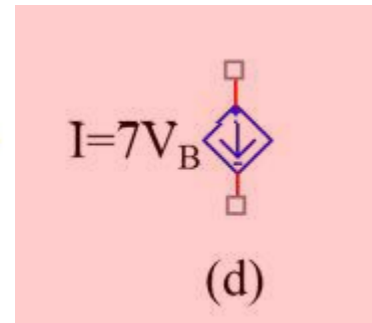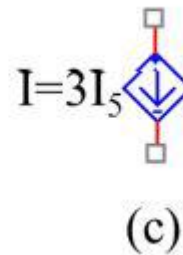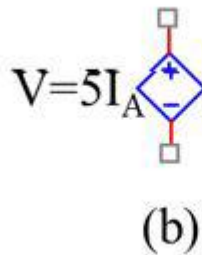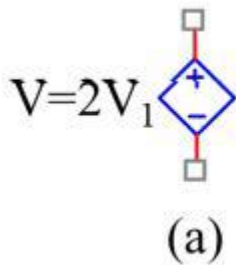
## Ideal Dependent Sources

$$I = 7V_B$$

where,  $V_B$  is measured somewhere else in the circuit.




# Sources

## Real Sources

What happens when you connect a **9 V** battery in parallel with a **1.5 V** battery as shown?

Applying KVL around this circuit seems to **fail!**

**What is wrong?**

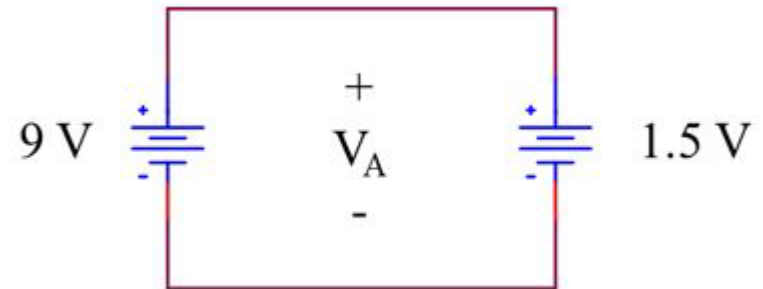




# Sources

## Real Sources

The problem is in **modeling** a **real source** using the previous circuit!

The chemical reaction inside the battery controls the rate of electrons that can flow between the terminals limiting the maximum current.

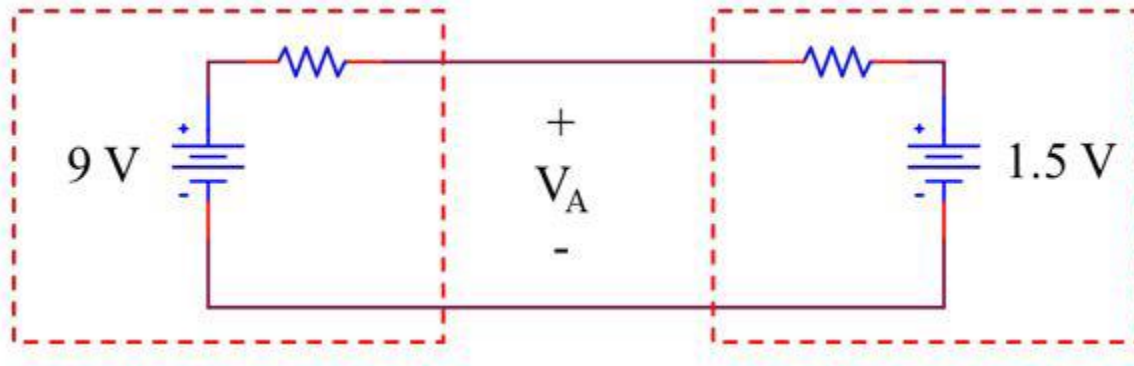
We model the effect of the chemical reaction as an **internal resistance**.



## Example Problems

### Example 6-1

For the circuit shown, the voltage across  $R_1$  is measured by an ideal voltmeter, and its value is found to be **30.5 V**. If the voltmeter is connected across the terminal bc. Determine the voltmeter reading ( $V_{bc}$ ).  
Determine the power consumed in each resistor.  
Determine the total power supplied by the voltage source.

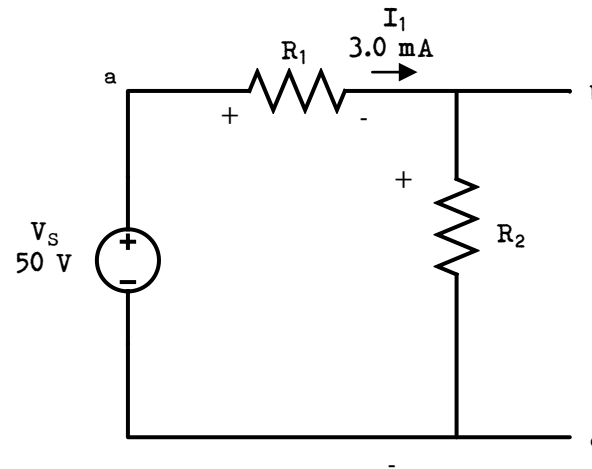


Example 6-1 will be explained on the whiteboard

## Example Problems

### Example 6-2

An electronic voltmeter with internal resistance ( $R_v$ ) of **10 M $\Omega$**  is used to measure the potential difference between node A and the ground of the circuit shown in the figure. The voltmeter reads **1 V**.

If the voltmeter is connected across the terminals of **R1**. What would be the voltage reading?

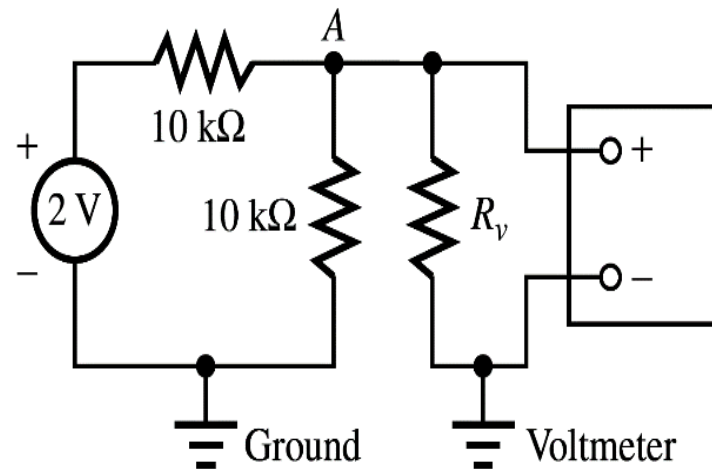

Example 6-2 will be explained on the whiteboard

## Example Problems

### Example 6-3

For the circuit shown, the following data is available:

$$V_S = 6\text{ V}$$

$$I_S = 31.935\text{ mA}$$


$$V_a = 4.258\text{ V}$$

$$P_1 = 30.343\text{ mW}$$

$$I_2 = 8.710\text{ mA}$$

$$I_5 = 10.645\text{ mA}$$

Calculate  $I_1$ ,  $I_3$ ,  $I_4$ , and the total power supplied by the source.

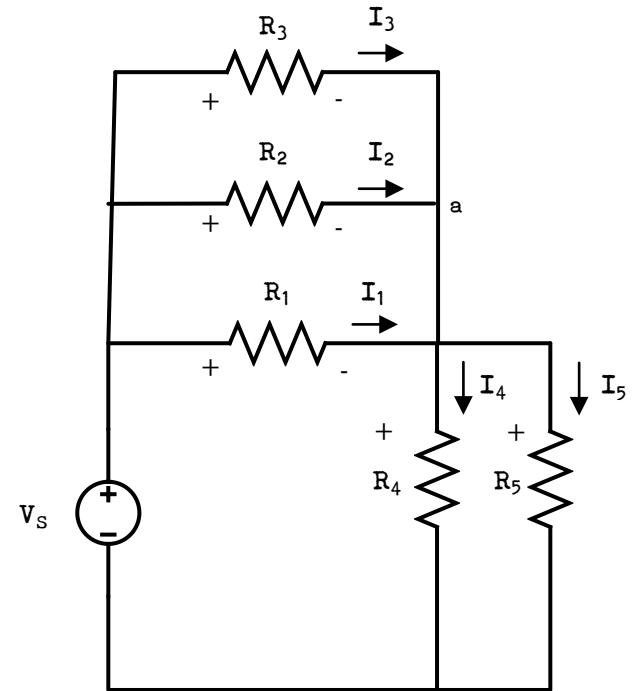

Example 6-3 will be explained on the whiteboard

**Additional notes will be given on the whiteboard**

## **References**

- [1] **Denise Thorson**, "Introduction to Electrical and Computer Engineering," University of Alaska Fairbanks, 2018.